

**II B.Tech I Semester Regular Examinations, March-2021**  
**Networks and Transmission Lines**  
**(Electronics and Communication Engineering)**


Time: 3 Hours

Max. Marks: 60


Note : Answer ONE question from each unit ( $5 \times 12 = 60$  Marks)

UNIT-I

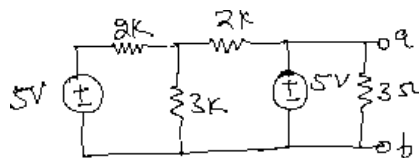1. a) Find the Thevenin's equivalent circuit for the following circuit across the terminal a and b [6M]




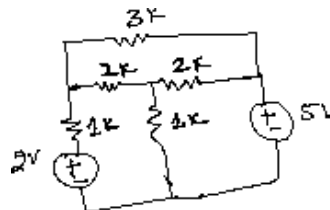- b) Find the current through each resistance of circuit shown below using nodal analysis. [6M]




(OR)

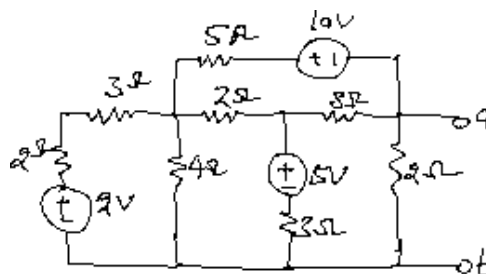2. a) Find the maximum power transferred by the source to the load of  $5\Omega$  load resistance. [6M]




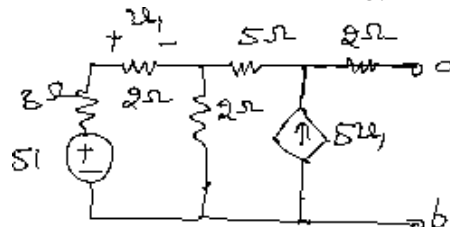- b) Find the Norton's equivalent across the terminals a-b. [6M]



**UNIT-II**

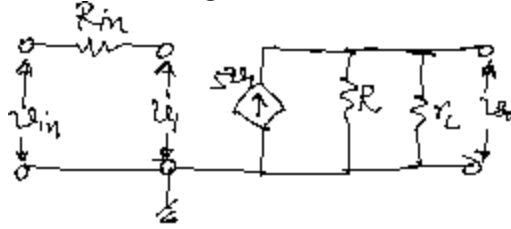3. a) Find the  $h$ -parameters of the following network. [6M]




- b) Two 2-port networks are connected in series and being represented by the  $[Z]$  and  $[Z]$  parameters as follows. [6M]

$$[Z] = \begin{bmatrix} 2 & 5 \\ 3 & 2 \end{bmatrix} \quad [Z] = \begin{bmatrix} 3 & 2 \\ 2 & 5 \end{bmatrix}$$


Find the  $h$ -parameters of the combined network.

**(OR)**

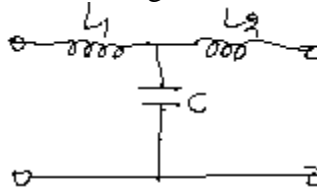4. a) Find The  $[Z]$  parameters of the following network. [8M]




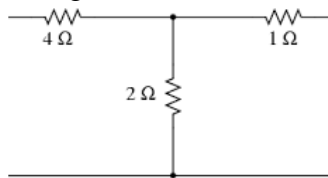- b) Find  $Z$  parameters of the following electrical network. [4M]




**UNIT-III**

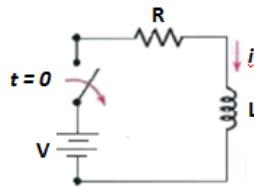5. a) Find the transient response of current in a series RL circuits for a DC excitation of  $V$  volts applied at  $t = 0$ . Assume inductor has zero initial energy. [8M]




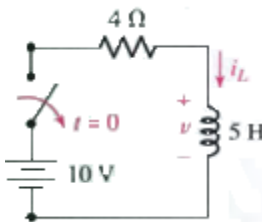- b) Write the expression of current through inductor in the following circuits. [4M]



**(OR)**

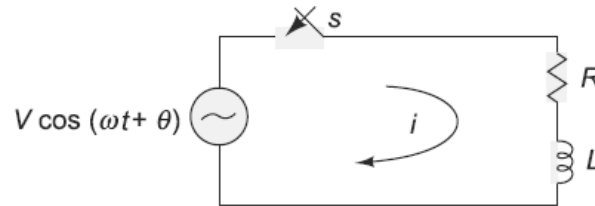6. a) Determine the complete solution for current 'i' in following circuit. [6M]



- b) The winding of an electromagnet has an inductance of 5 H and a resistance of 20 Ohms. When it is connected to a 220 V, DC. supply, calculate: [6M]
- the steady state value of current flowing in the winding,
  - the time constant of the circuit,
  - the value of the induced e m f. after 0.2 s,
  - the time for the current to rise to 90% of its final value, and
  - the value of the current after 0.5 s

#### UNIT-IV

7. Starting from the electrical equivalent circuit, derive the voltage and current expressions at any point on transmission line. Write the same for infinite transmission line. [12M ]

(OR)

8. a) What is the difference between the distortions less and loss less transmission? Please give example of each type transmission line. [8M]
- b) Explain the requirements for distortion less transmission on transmission lines [4M]

#### UNIT-V

9. a) Derive the expression for input impedance of a transmission line of length  $l$  and characteristic impedance  $Z_0$ . [6M]
- b) Find the input impedance of a short circuited and open circuited transmission line. Also draw the it's behavior in respect to the time scale. [6M]

(OR)

10. a) What do you mean by the impedance matching? Explain the impedance matching using stub. [8M]
- b) Find the reflection coefficient and standing wave ratio of a transmission line if it is terminated at the short circuit and open circuit load. [5M]

\*\*\*\*\*